



Air University
(Final-Term Examination: Spring 2024)

Subject: Digital Logic Design
Course Code: EE-123
Class: BS-CYS
Semester: II
Section: A & B

Total Marks: 100
Date: 8th June, 2024
Time: 13:30-16:30
Duration: 2 Hours
FM Name: Dr. Bahman R. Alyaei

HoD Signatures: _____

FM Signatures: _____

Note:

- This is closed book exam, All questions must be attempted.
- This examination carries 45% weight towards the final grade.
- Calculators are not allowed

Q. No. 1 (CLO 3)		25 Marks																																								
a	For the following Boolean expressions Draw the logic circuit diagram using appropriate logic gates: 1) $X = A(BC)$. 2) $Y = (A + B)C$.	10																																								
b	Apply the rules of Boolean Algebra to Evaluate the standard POS expression for the following digital system. $Z = (A + B + \bar{C})(A + C)$	5																																								
c	Apply the method of Numerical Expansion to generate the Standard SOP form of the following Boolean Expression. $M = \bar{A} + A\bar{B} + ABC$	5																																								
d	Using rules of Boolean Algebra, Express the equation of the following digital system in minimum form. $N = A + AB + \overline{(A + AB)}C$	5																																								
Q. No. 2 (CLO 3)		30 Marks																																								
a	For the truth table shown, Evaluate the following: (i) The standard SOP expression of the output variable. (ii) The standard POS expression of the output variable. (iii) The simplified SOP expression of the output variable using K-Map. <table><tr><th colspan="3">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>x</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>x</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	Inputs			Output	A	B	C	X	0	0	0	1	0	0	1	x	0	1	0	0	0	1	1	1	1	0	0	1	1	0	1	x	1	1	0	0	1	1	1	1	5+5+10
Inputs			Output																																							
A	B	C	X																																							
0	0	0	1																																							
0	0	1	x																																							
0	1	0	0																																							
0	1	1	1																																							
1	0	0	1																																							
1	0	1	x																																							
1	1	0	0																																							
1	1	1	1																																							
b	For the non-standard Boolean expression given below, Generate the truth table. $X = \bar{A} + AB$	10																																								

	Q. No. 3 (CLO 4)	25 Marks
a	<p>Using the method of Truth Table and word comparison (not bit by bit method), Design the two bit word comparator that produces the following output:</p> <ol style="list-style-type: none"> 1) Equal. 2) Greater than or equal. 3) Less than or equal. <p>Note: Strict greater and less is not required.</p>	5+10+10
	Q. No. 4 (CLO 4)	10 Marks
a	<p>Design the following digital systems using block level design method.</p> <ol style="list-style-type: none"> 1) Four bit adder using the blocks Full-Adder. 2) Four bit Multiplier using blocks of 4-bit adders and necessary logic gates. 	5+5
	Q. No. 5 (CLO 4)	10 Marks
a	<p>Design the following digital systems using appropriate MUX blocks.</p> <ol style="list-style-type: none"> 1) Using appropriate Multiplexer (MUX) block, design the following digital system. $Y = \overline{A_2}A_1A_0 + A_2\overline{A_1}A_0 + A_2A_1\overline{A_0}$ 2) Using 8×1 MUX with Enable (EN) input and necessary logic gates, implement 16×1 MUX. 	5+5

***** End of Question Paper *****